

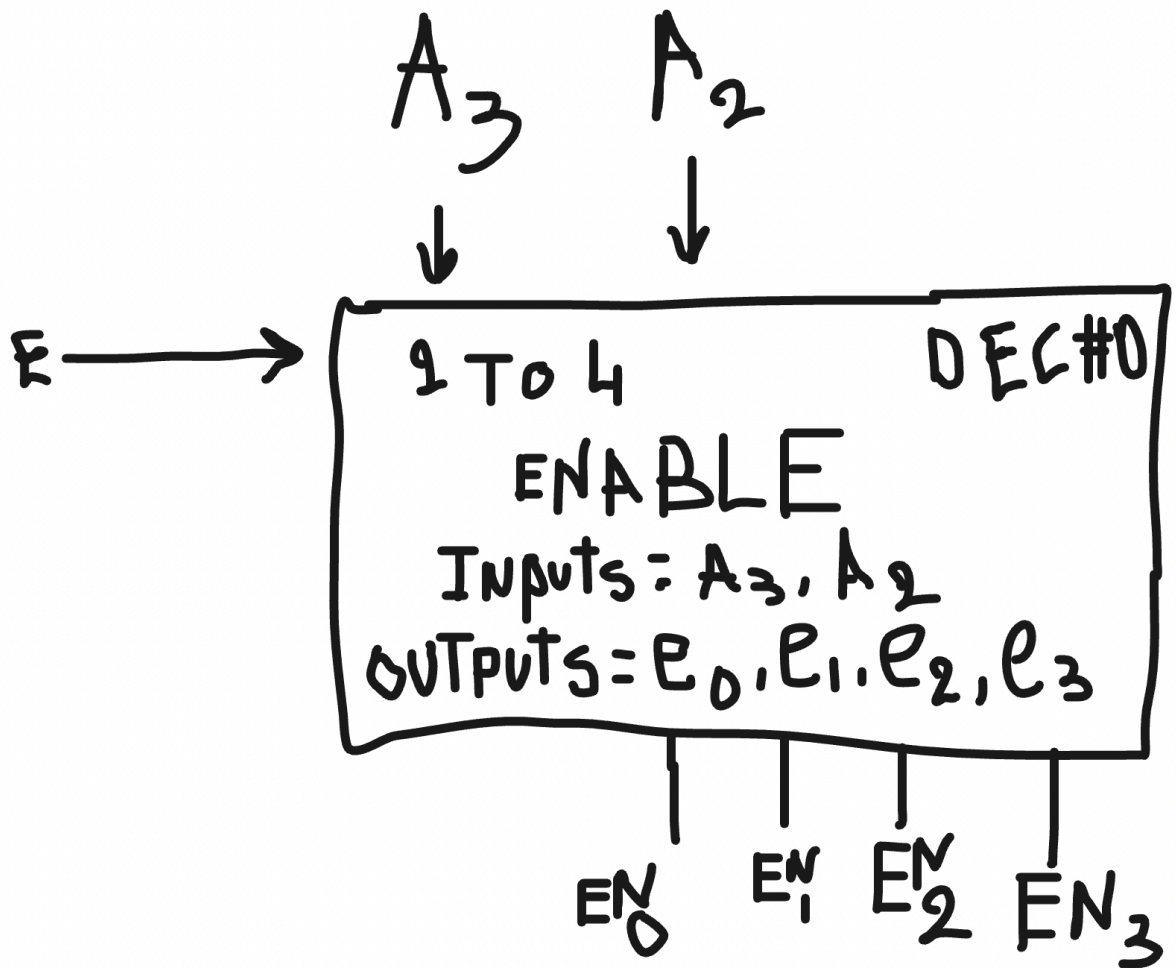



Harder Problem 1

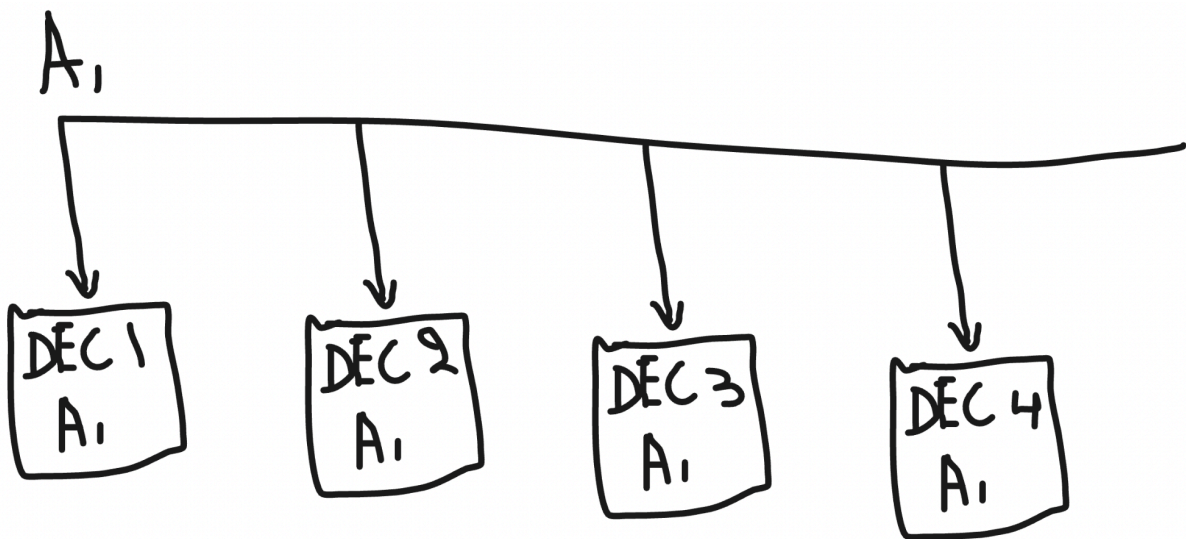

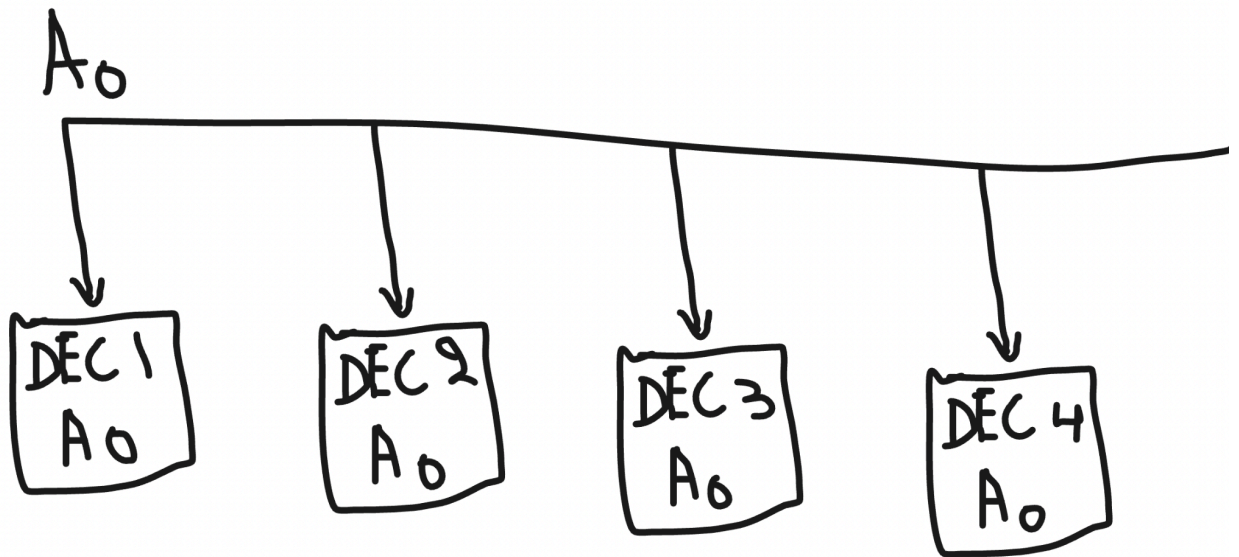

Harder Problem 2
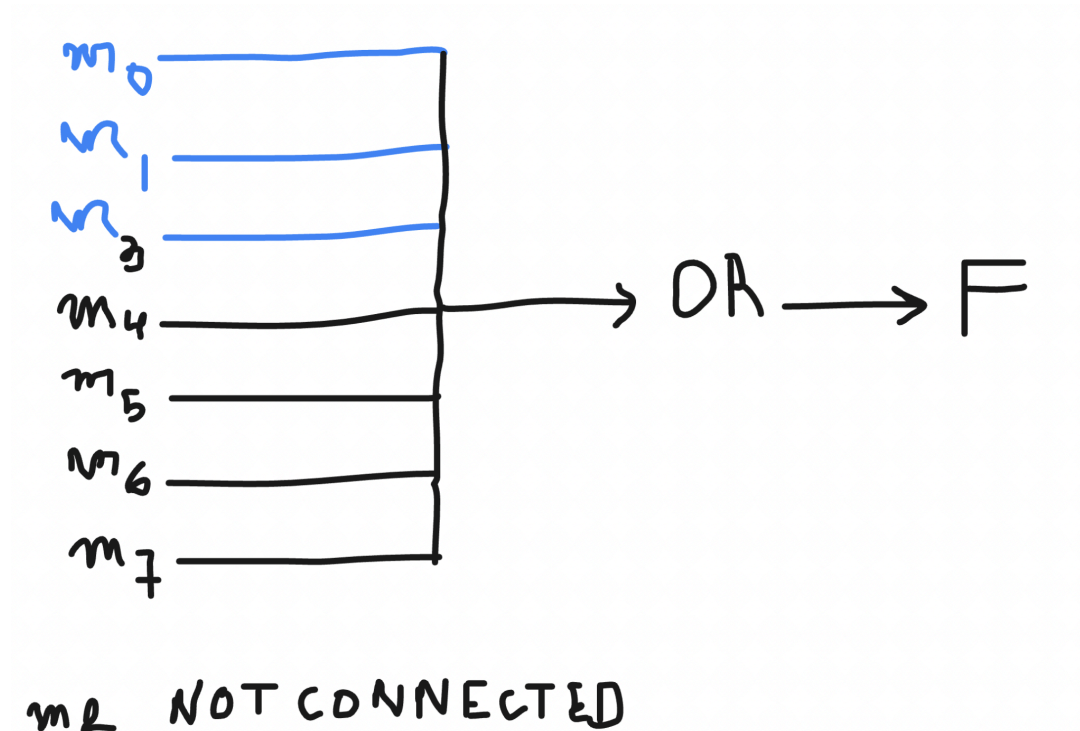
$$F = m_0 + m_1 + m_3 + m_4 + m_5 + m_6 + m_7$$



Harder Problem 3

so we assume A is the MSB and D is the LSB of ABCD.

$$NSL = A' B C D'$$




$$NSH = A + B C D$$

$$EWL = A B C D'$$

$$EWH = A' + B C D$$

+ = OR, adjacency = AND, and ' = NOT

Harder Problem 4

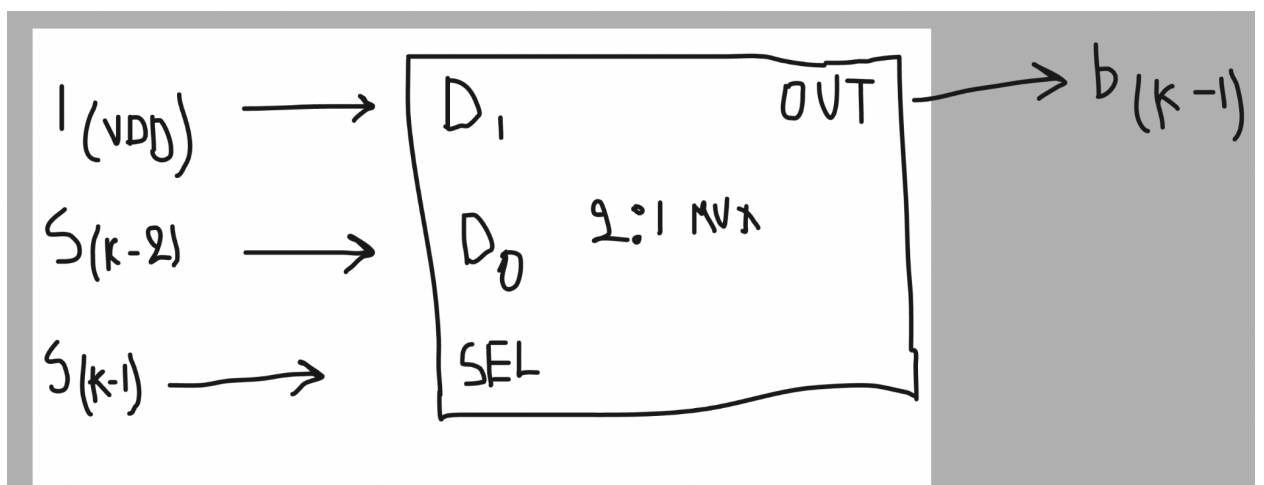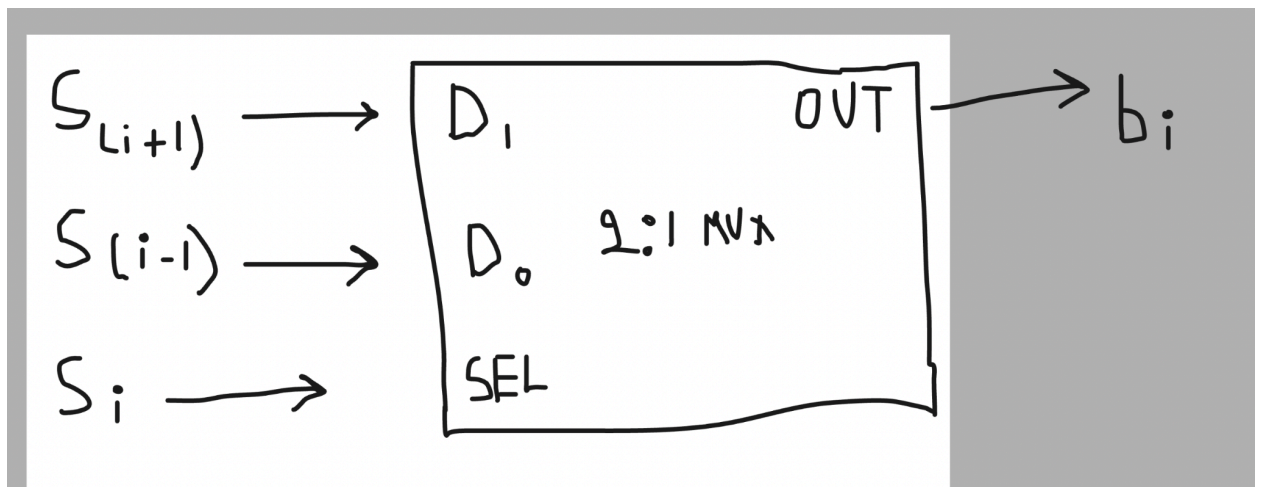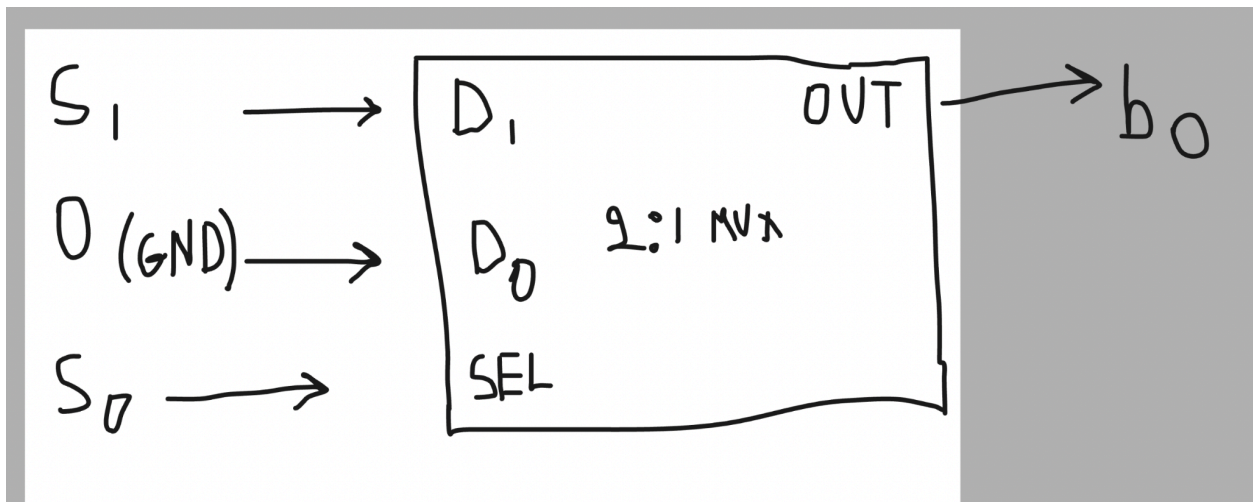

Harder Problem 5:

5(a):

so output bit name i'll call it $T[i]$, $T[i] = (S[i] \text{ AND } S[i+1]) \text{ OR } (S[i-1] \text{ AND NOT } S[i-2])$, so $T[i] = (S[i] \& S[i+1]) \mid (S[i-1] \& \sim S[i-2])$

5(b): simplified equation: $T[i] = (S[i] \text{ AND } S[i+1]) \text{ OR } (S[i-1] \text{ AND NOT } S[i-2])$ so $T[i] = (S[i] \& S[i+1]) \mid (S[i-1] \& \sim S[i-2])$

5(c): simplified is $T[i] = S[i] \text{ OR NOT } S[i-2]$

5(d): $T[0] = S[0] \text{ AND } S[1]$ so $T[0] = S[0] \& S[1]$

the output bit $T[1]$ is $T[1] = S[0] \text{ OR } (S[1] \text{ AND } S[2])$

output bit $T[k-1]$ is $T[k-1] = S[k-2] \text{ AND } (S[k-1] \text{ OR NOT } S[k-3])$